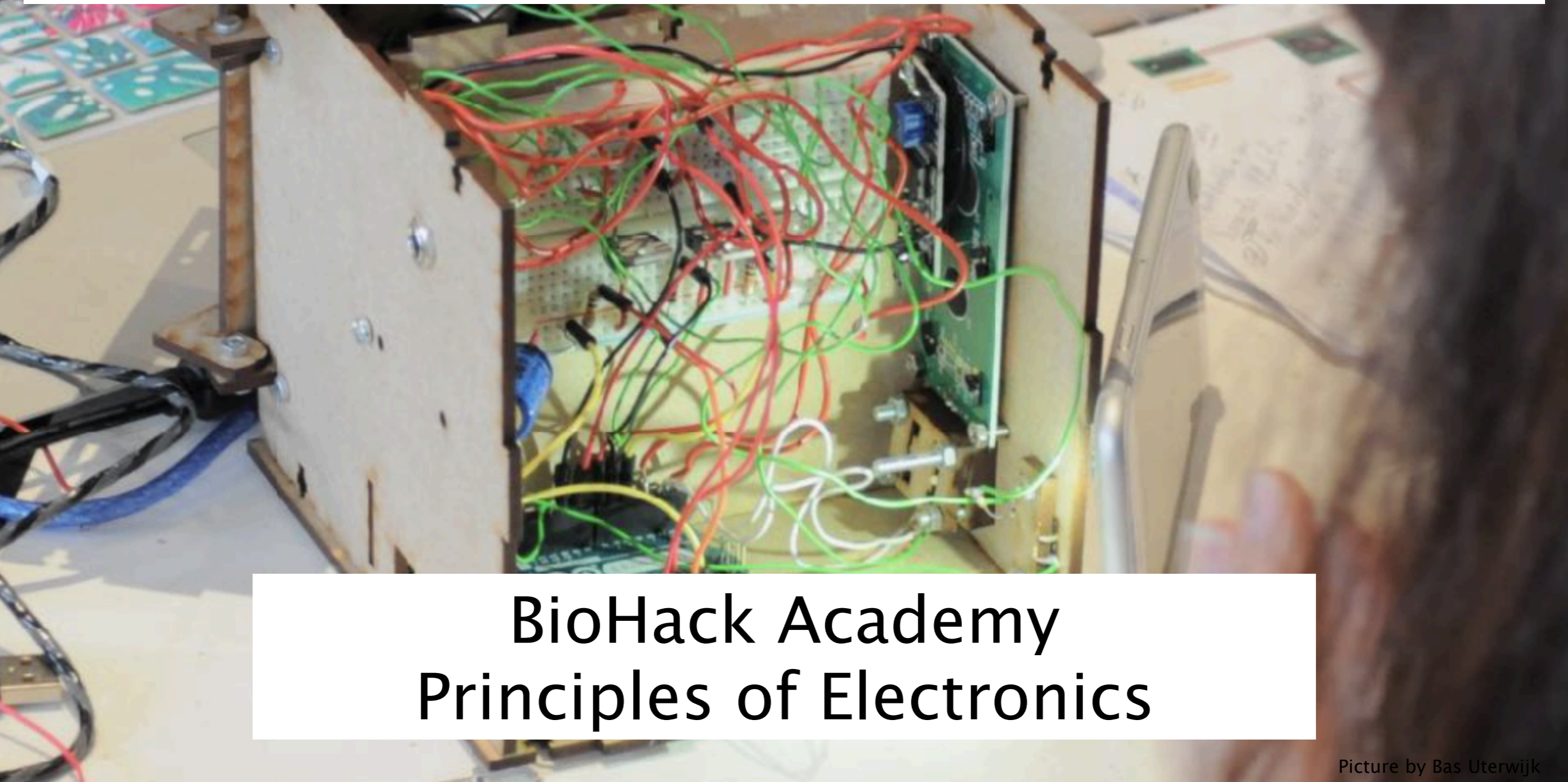


biohack academy  
**waag society**



# BioHack Academy Principles of Electronics



# A circuit


A circuit is a **CLOSED LOOP** in which electrons can flow.

Electrons flow = Current

How can I generate a Current?

By connecting two electrodes of a battery

For example: Battery + Resistor

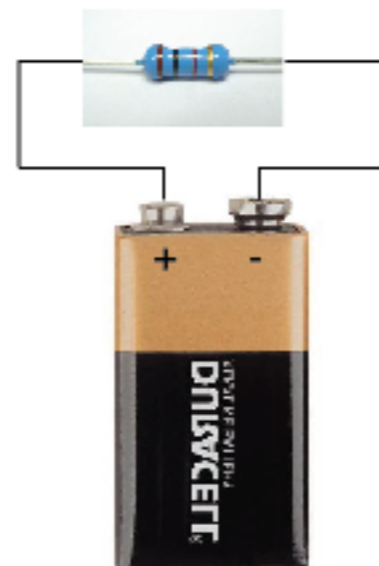



# Battery



The battery is the power supply of our circuit.

It has two sides:

- + a.k.a. Plus, VCC, V+ or +V
- - a.k.a. Minus or GND

Unit of measure is Volt (V).

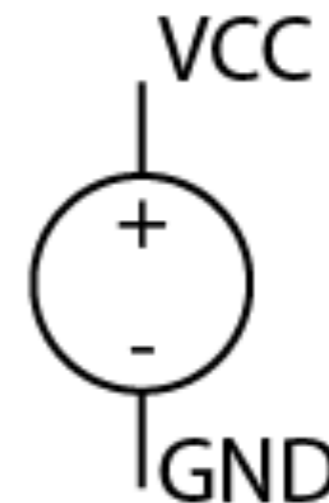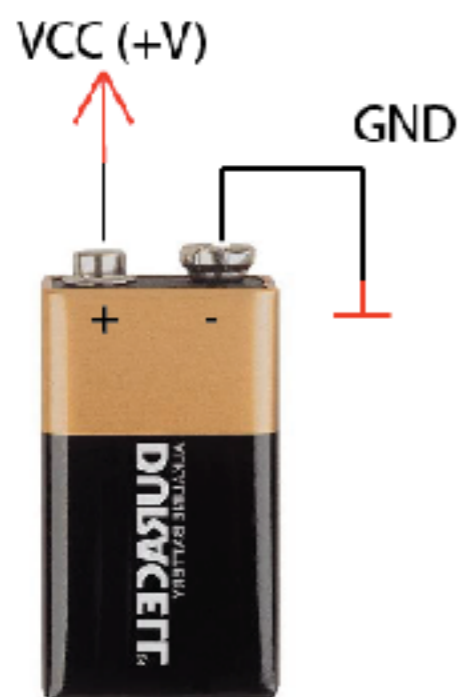Voltage:  
It's the difference in potential between two points





# Batteries & Power Supplies

VCC = 9V



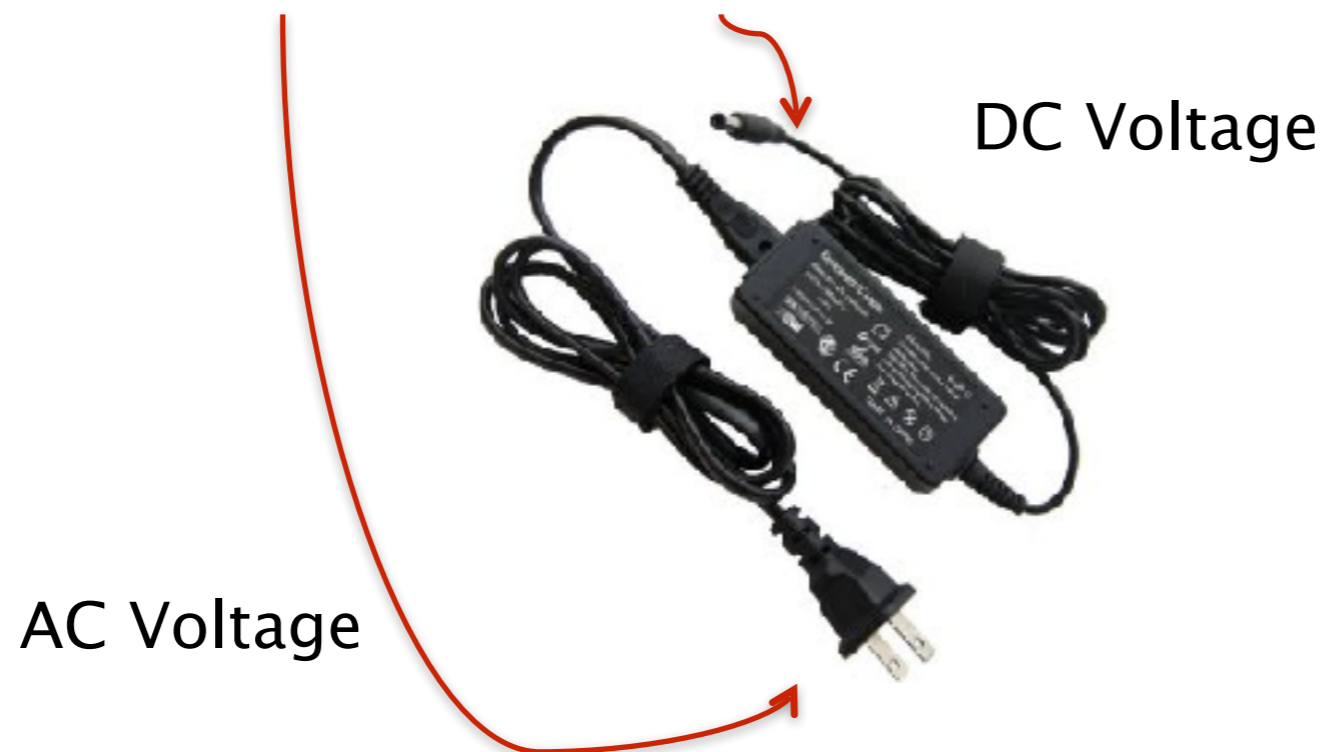
1.5V



3V



From the grid (220V) to 12V (the output that be different), VCC = 12V.





# Resistor

It has two sides




The orientation is irrelevant

Unit of measure is Ohm ( $\Omega$ )






# A basic circuit

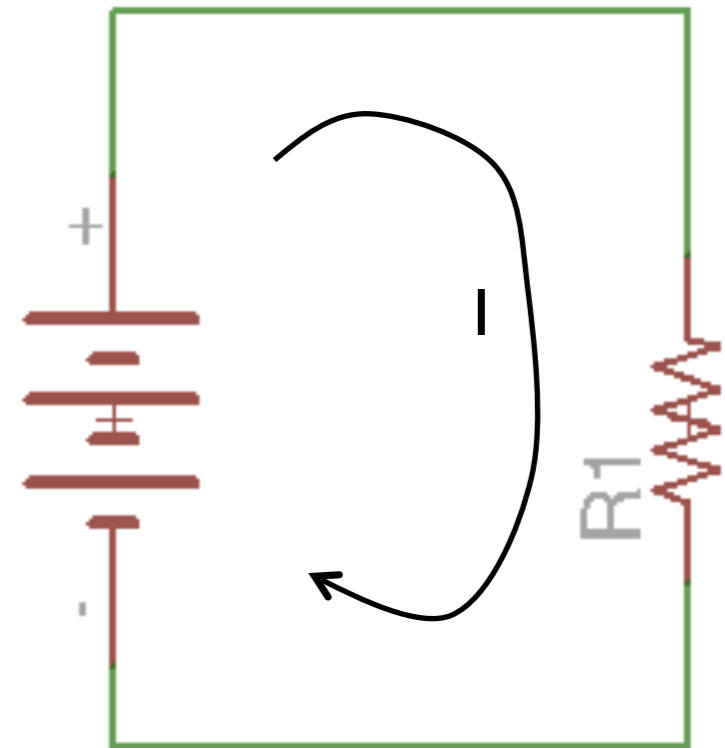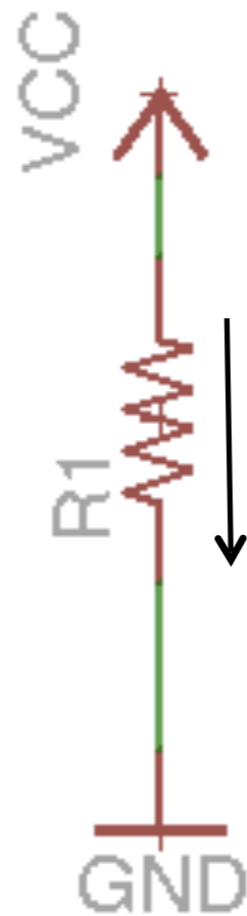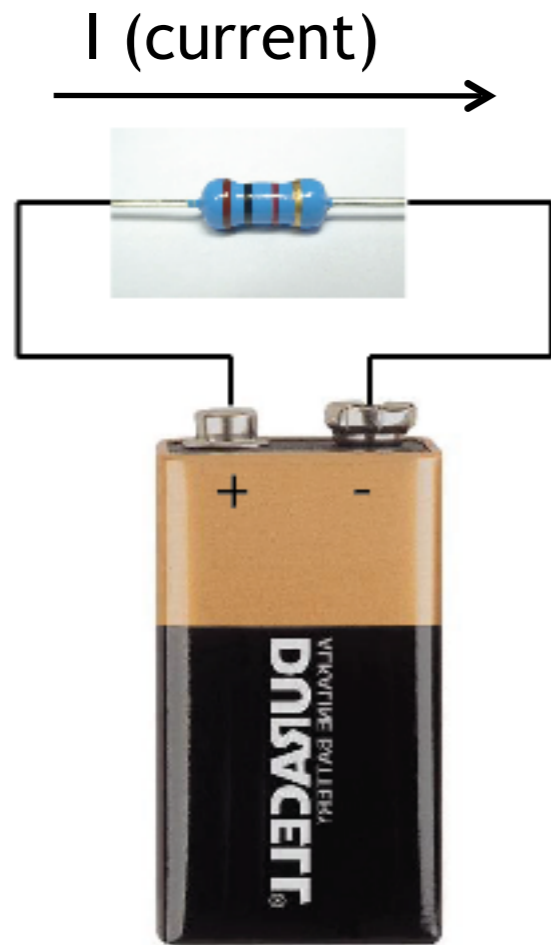

- **Voltage:** is the difference in potential between two points
- **Current:** is the rate at which charge is flowing
- **Resistance:** is a material's tendency to resist the flow of electrons / current




# A basic circuit

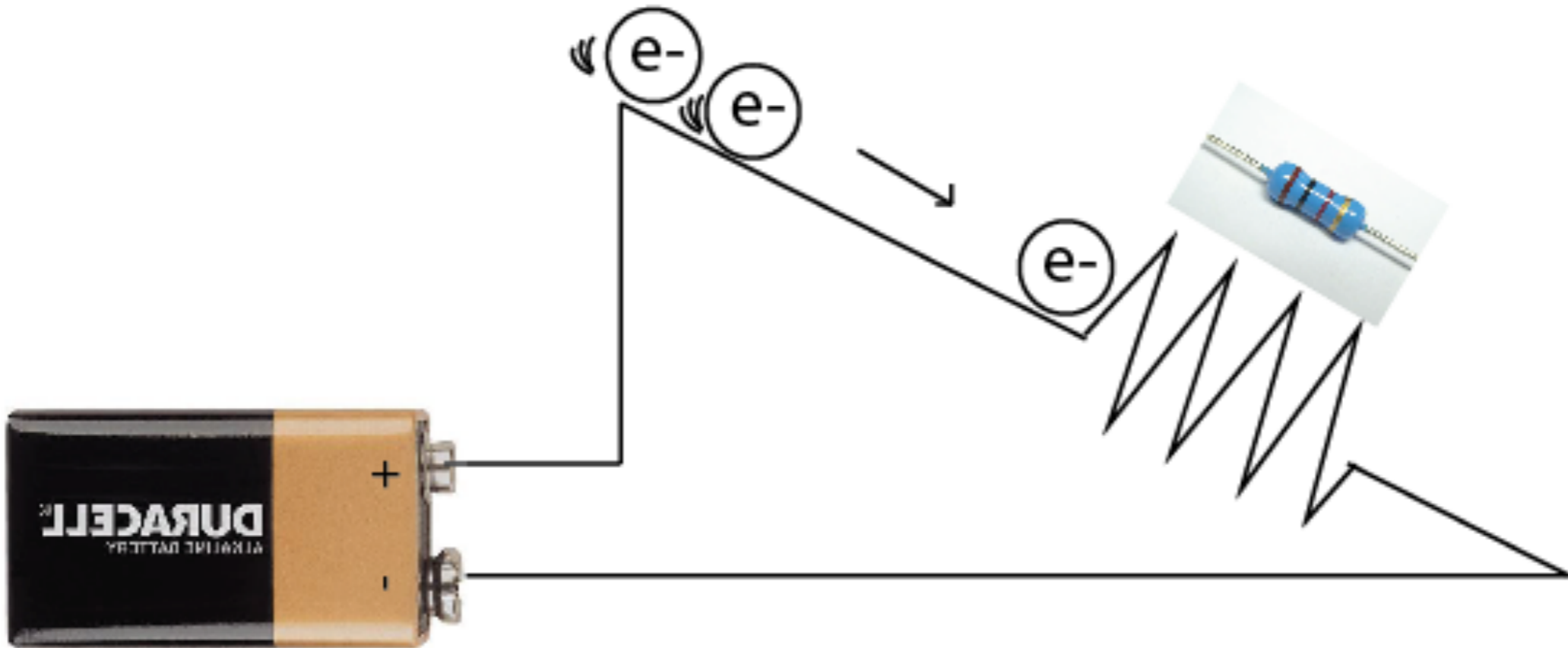



# Electricity vs Waterfall

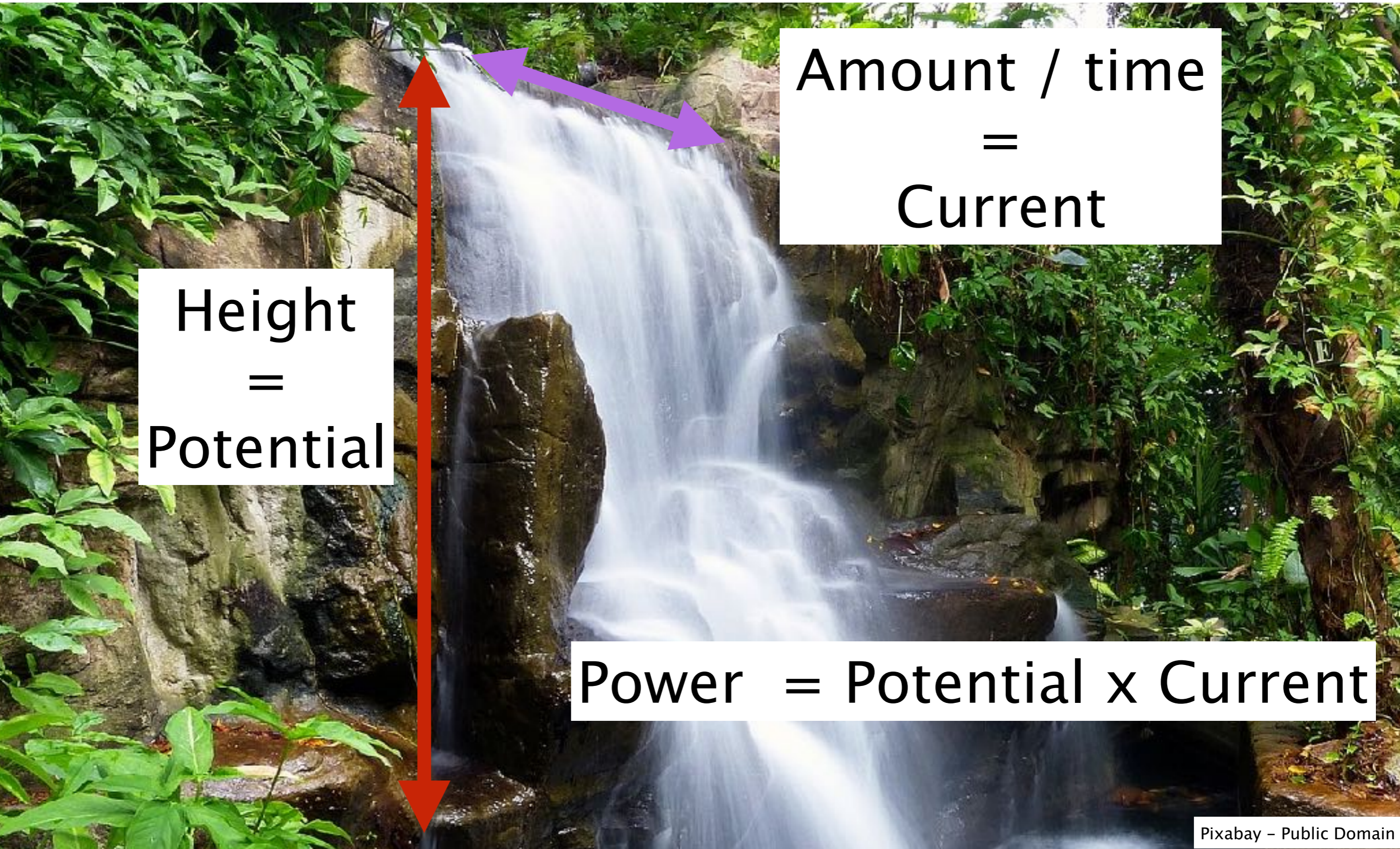

Amount / time  
=  
Current


Height  
=  
Potential

Power = Potential x Current






# Ohm's Law

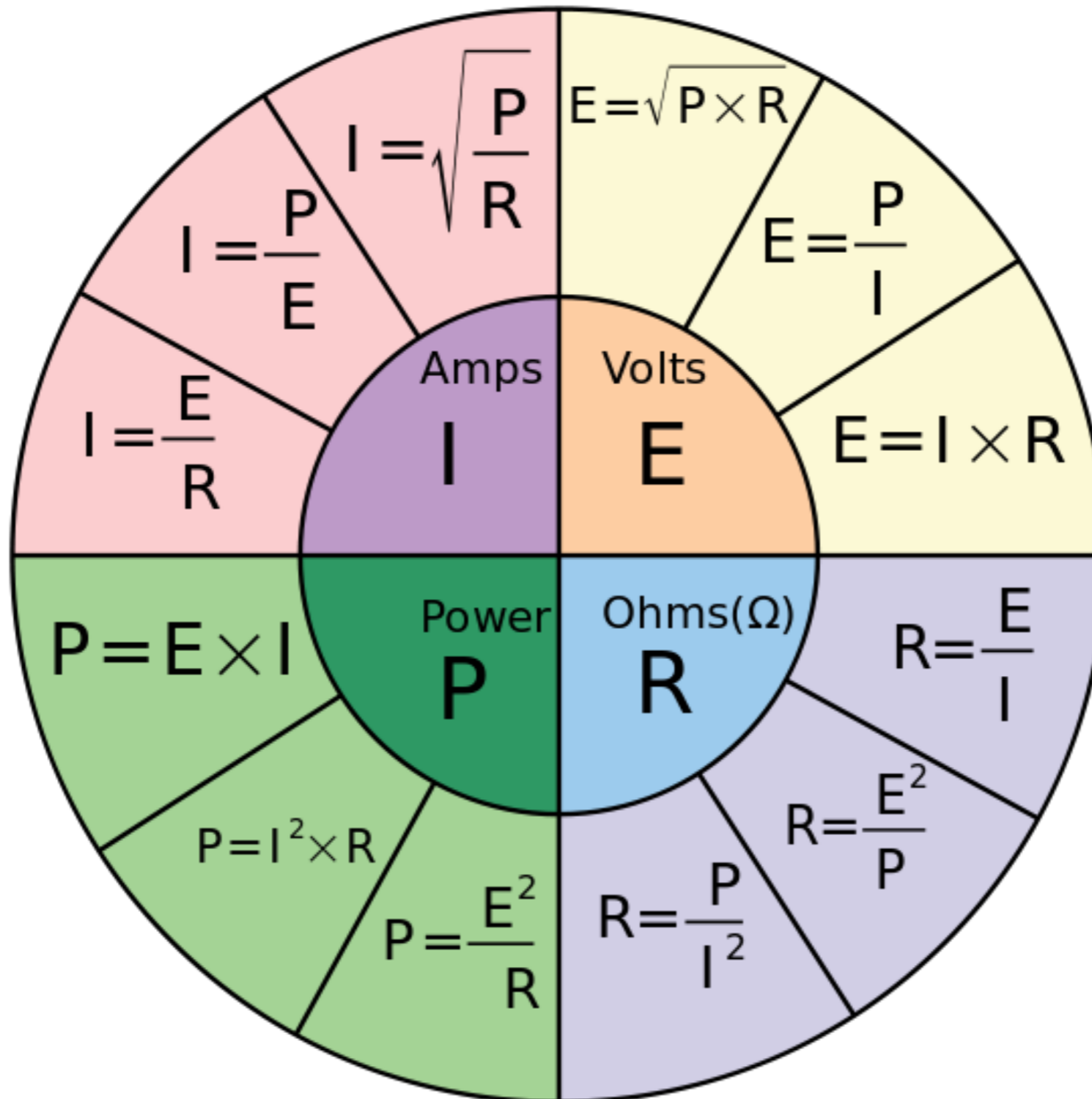



# Using Ohm's Law

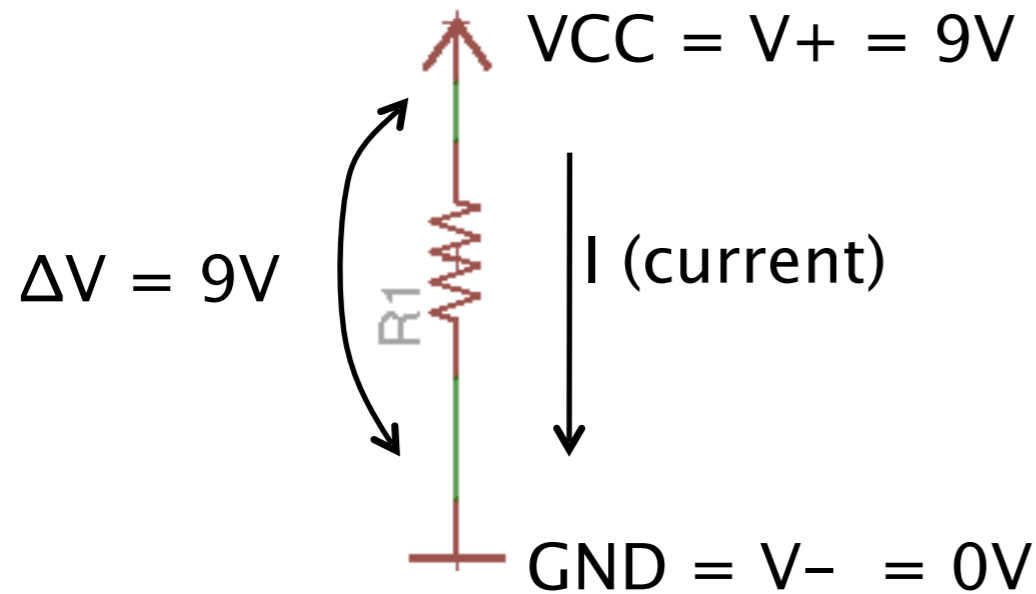

## Ohm's Law

$$\Delta V = (V+) - (V-) = R * I$$

$$V = RI$$

$$I = V/R$$

$$R = V/I$$

Ex 1: Calculate the Current

$$V = 9V$$

$$R1 = 1k\Omega = 1000\Omega$$

$$I = V/R = (VCC - GND) / I = (9V - 0V)/1k\Omega = 9mA = 0.009 A$$

Ex 2: Calculate Resistance

$$V = 3V$$

$$I = 20mA$$

$$R = V/I = 3V/20mA = 150\Omega$$




# Measuring

Potential



Current

Resistance

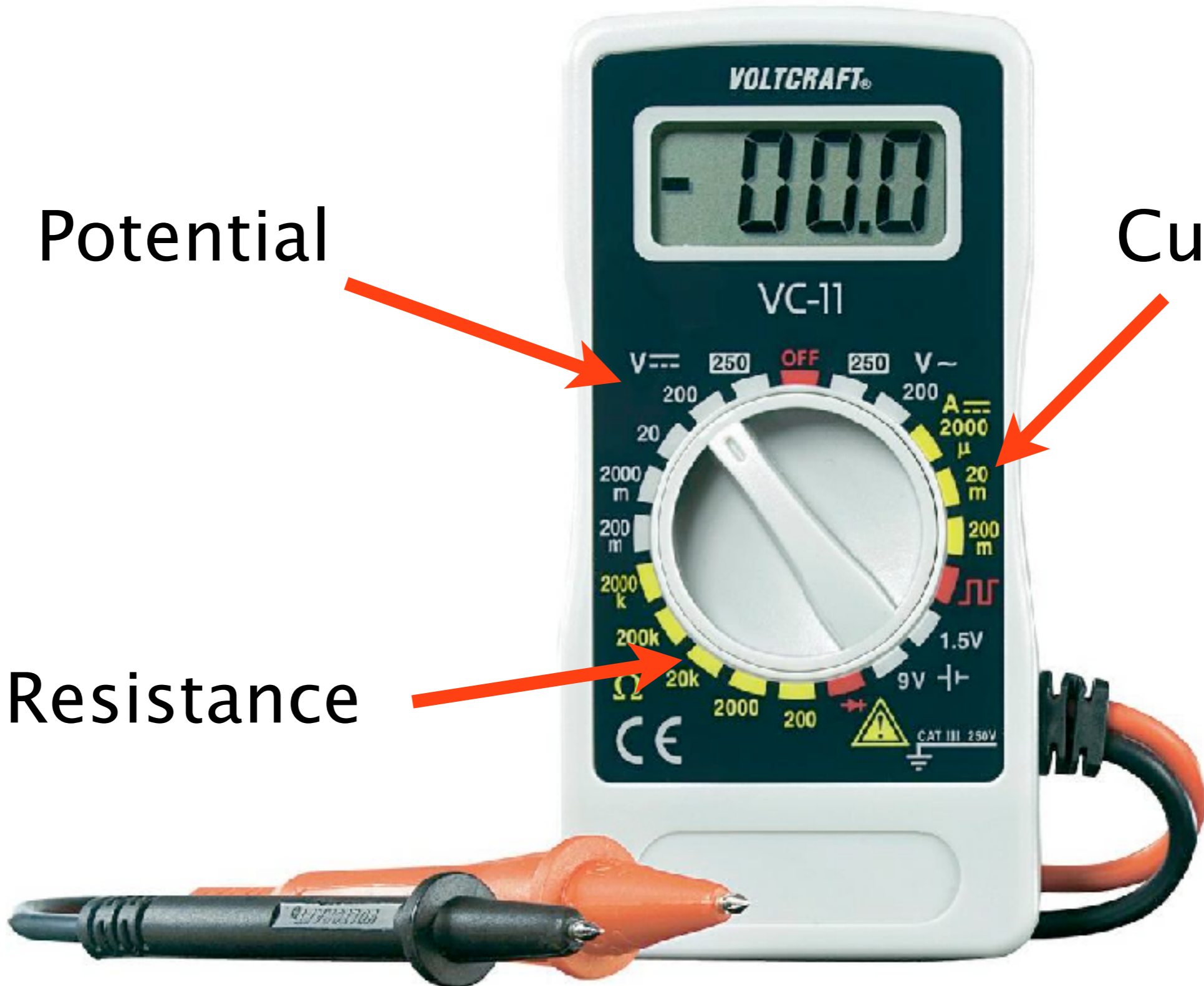



# Breadboard

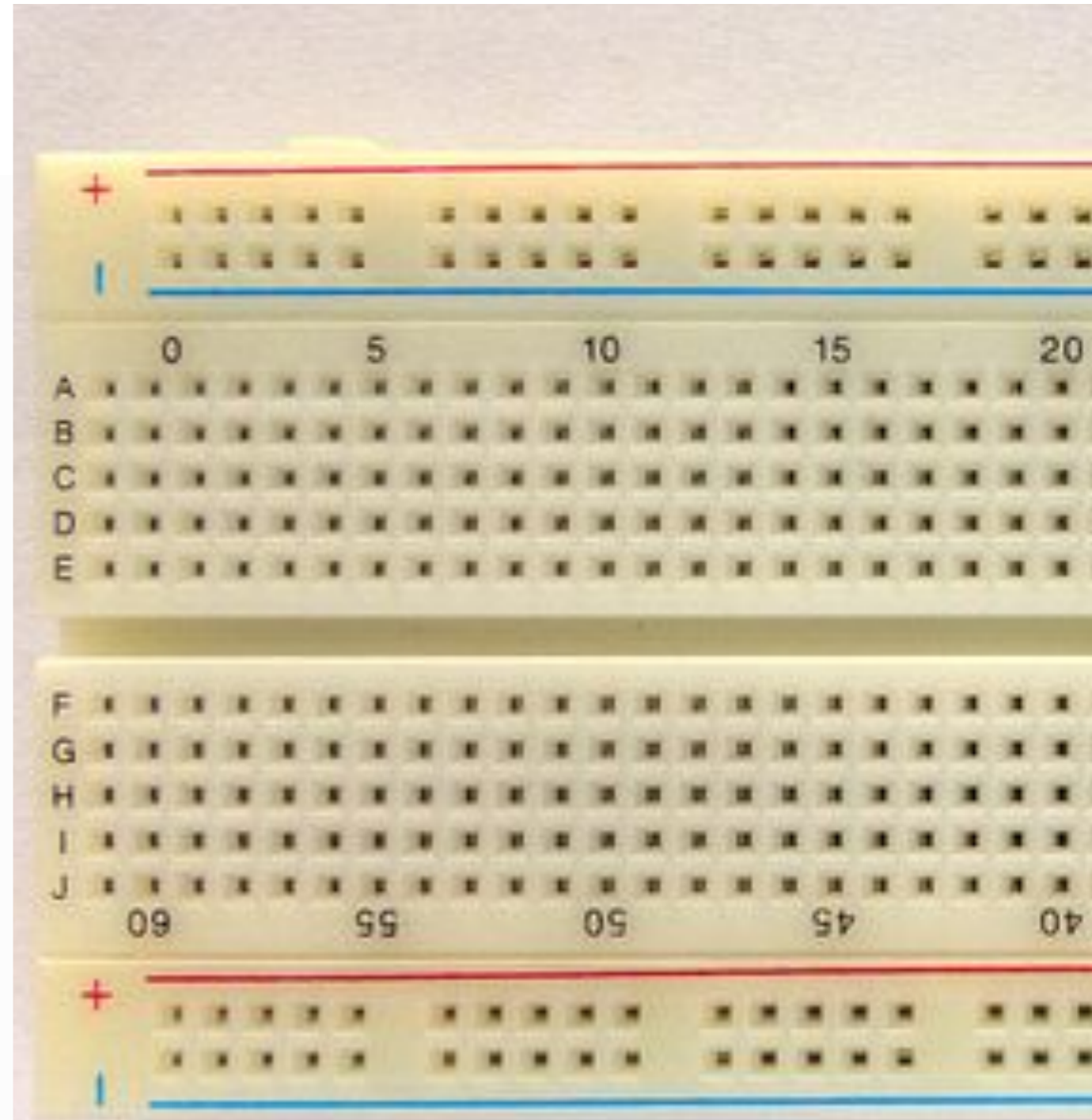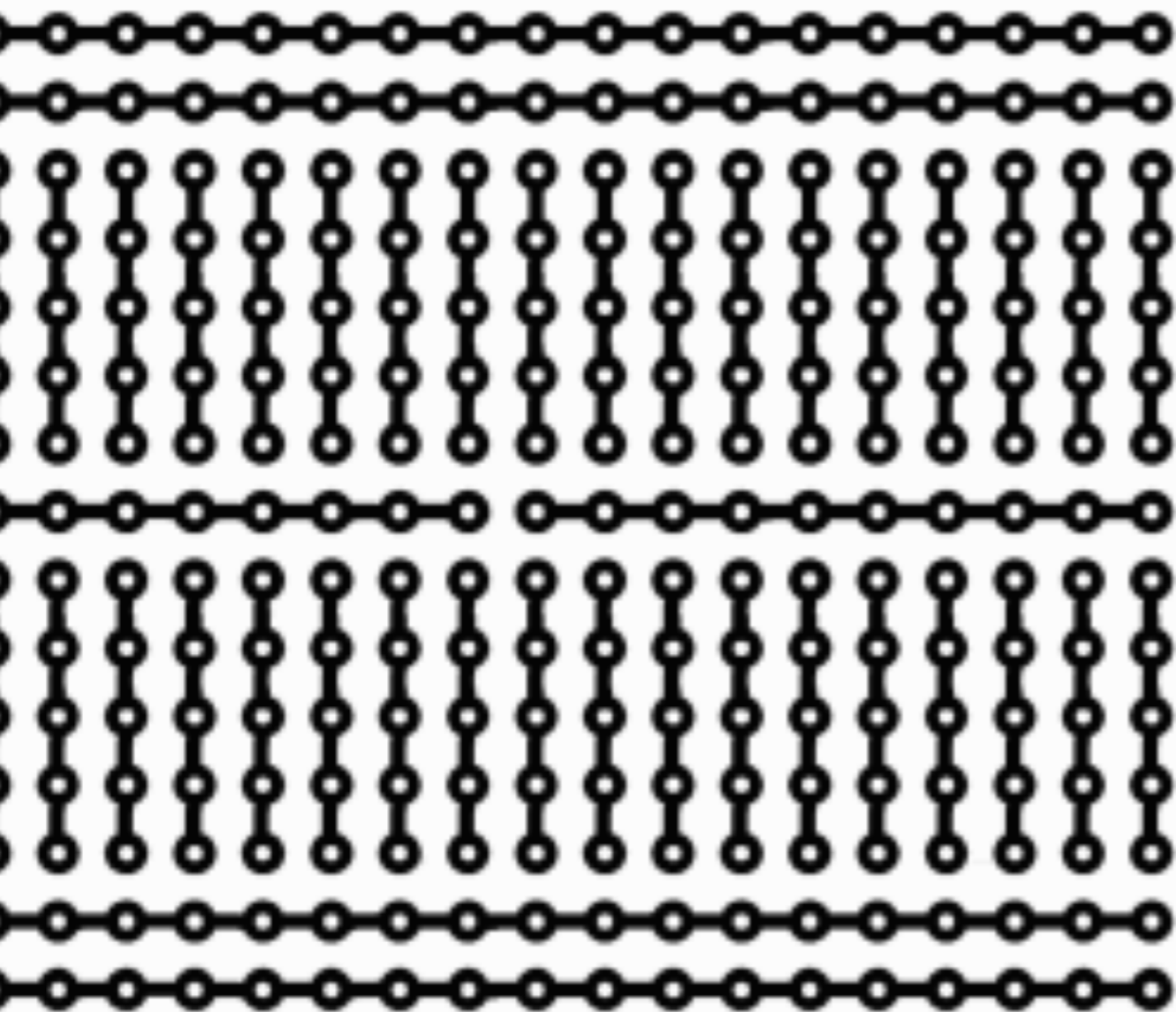



**waag society**

institute for art, science and technology

# Soldering




# Soldering Iron – 350 C






# Soldering is easy


Good join

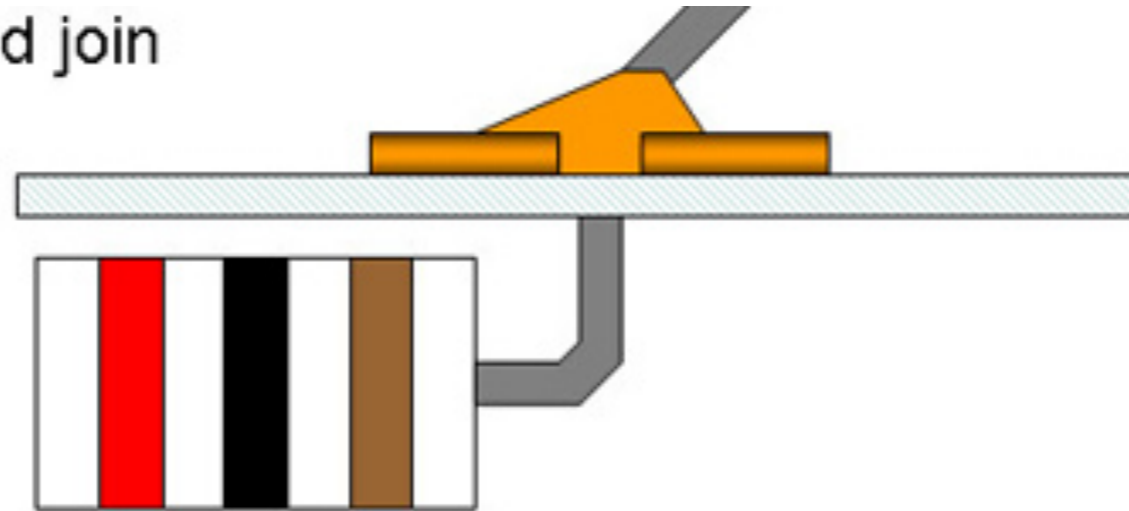

Bad join

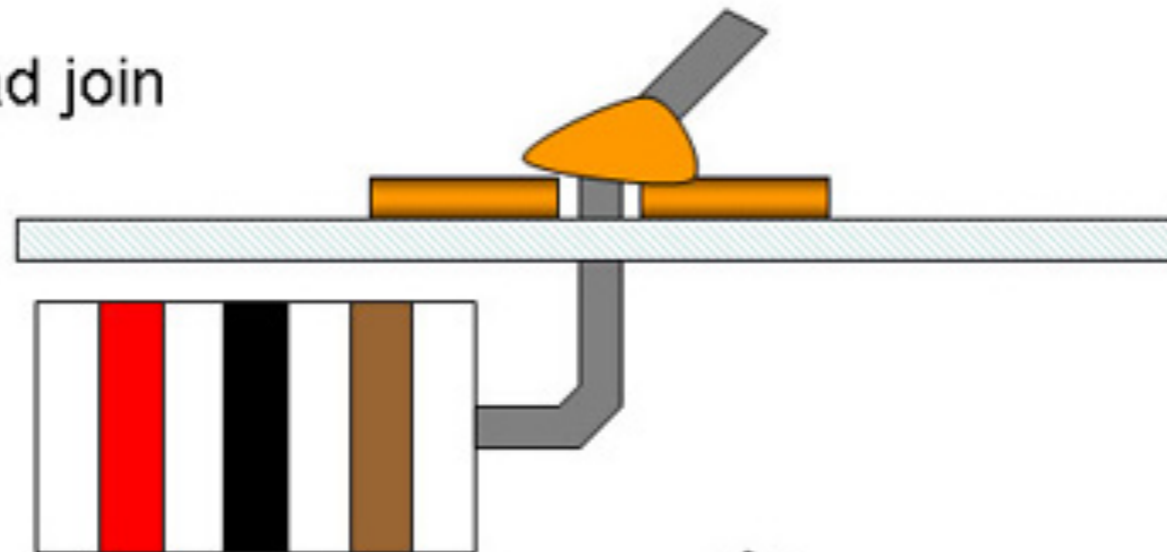

Bad join

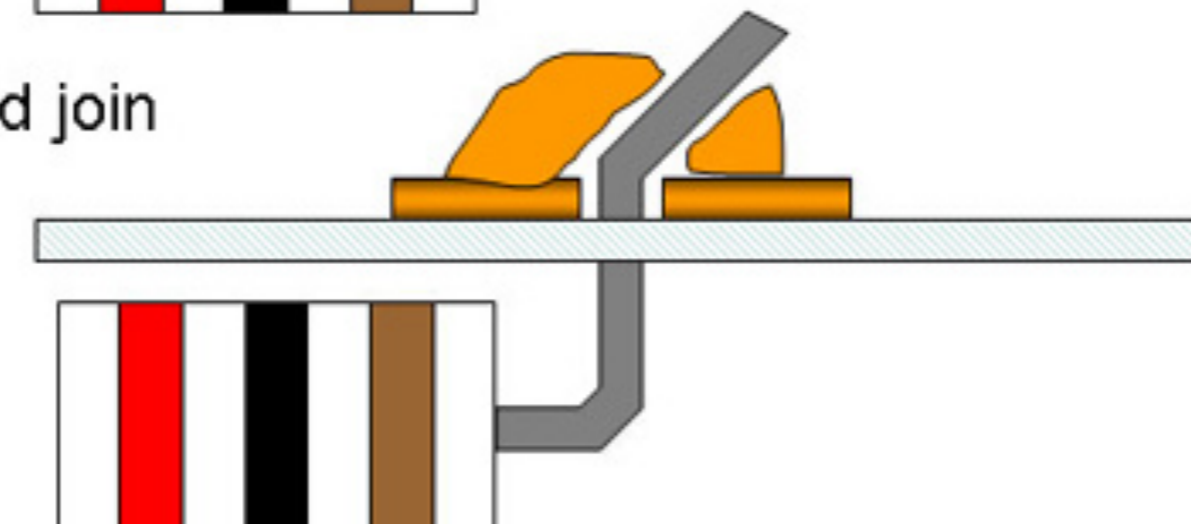



**waag society**

institute for art, science and technology

# Electrical Safety





Remember what your mother told you

**DANGER**

**220 VOLTS**



## Dangers:

- High voltage
- Low resistance  
=
- High Current
- Make use of isolation!
- Better safe than sorry!





**some  
rights  
reserved**